

Lab 1 – Device Characterization and Biasing Circuits

Joey McIntyre – 400520473 – mcintj35

ELECENG 3EJ4 – Electronic Devices and Circuits II

Dr. Chih-Hung Chen

Sunday, September 21st, 2025

Part 1: DC Characterization of an NPN-BJT 2N3904

A) SPICE Simulation

1.1

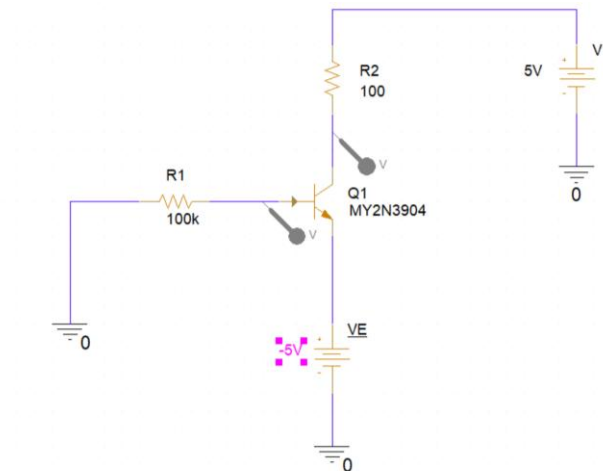


Figure 1: PSpice schematic diagram used to characterize a NPN-BJT 2N3904

1.2

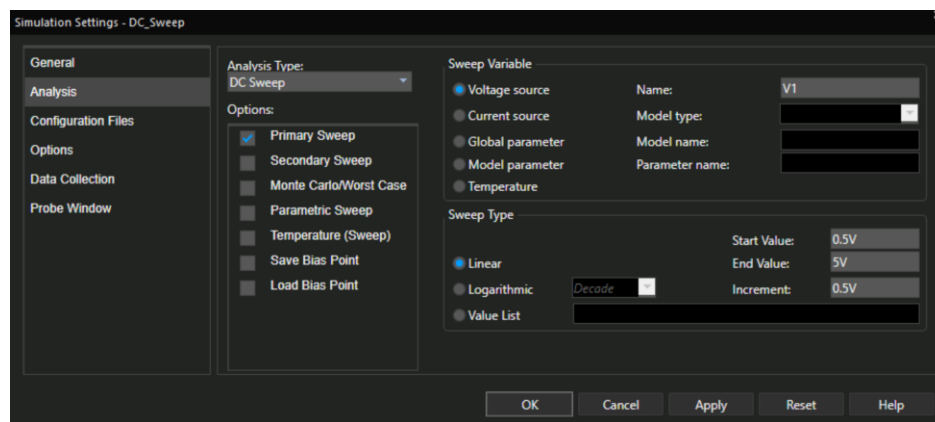


Figure 2: PSpice simulation settings used for DC sweep

1.3: The V_A represents the early voltage which is a measure of the output resistance of a BJT in the active region. By observing the definition of V_A in Fig. 6.18 of the textbook, I was able to calculate the V_A from the I_C vs. V_{CE} plot in excel using the equation of the trendline to solve for the intercept by setting $I_C = 0$:

$$\begin{aligned} I_C &= mV_{CE} + b \\ 0 &= mV_{CE} + b \\ V_{CE} &= -\frac{b}{m} \Rightarrow V_A = \frac{b}{m} \end{aligned}$$

B) AD3 Measurement

1.5



Figure 3: Experimental setup for the DC characterization of an NPN-BJT 2N3904

C) Questions for Part 1

For the NPN-BJT 2N3904 characterized, if we want to bias this device to conduct a collector current $I_C \approx 1.0$ mA at the lowest V_{CE} value, answer the following questions.

Q1. (7 Points): Based on the simulated data in Steps 1.2-1.4, use the bias condition giving the closest I_C value to the desired collector current, find out:

V+ (VCC)	V- (VE)	V(Q1C) (Volt)	V(Q1B) (Volt)	VCE (Volt)	VBEon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = I_C/I_B$	VA (V)	ro=VA/IC	gm = IC/25mV	r π = 25mV/IB
0.5	-1.5	0.397558296	-0.878689331	1.898	0.621	100	1.00E+05	1.02E-03	8.79E-06	117	1000	9.76E+05	4.10E-02	2845

Figure 4: Closest I_C to 1.0 mA at the lowest V_{CE} Value

(1) What are the simulated V_{BEon} in volts and the base current I_B in μA ?

$$V_{BEon} = 0.621 \text{ V}, I_B = 8.79 \times 10^{-6} \text{ A} = 8.79 \mu A$$

(2) What is the $\beta = I_C/I_B$ value at this I_C ?

$$\beta = \frac{I_C}{I_B} = 117$$

(3) What is the early voltage $|V_A|$ in volts?

$$|V_A| = 1000 \text{ V}$$

(4) What is the output resistance r_o in $k\Omega$?

$$r_o = \frac{V_A}{I_C} = 9.76 \times 10^5 \Omega = 976 \text{ k}\Omega$$

(5) What is the transconductance g_m in mS?

$$g_m = \frac{I_C}{25mV} = 4.10 * 10^{-2} \frac{A}{mV} = 41 mS$$

(6) What is the input resistance r_π in $k\Omega$?

$$r_\pi = \frac{25mV}{I_B} = 2845 \frac{mV}{A} = 2.845 k\Omega$$

Q2. (8 Points): Based on the measured data in Step 1.8, use the same bias condition found in Q1 (or the first reliable data if that bias condition is an outlier), find out:

V+ (VCC)	V- (VE)	Channel 1 (VC)	Channel 2 (VB)	VCE (Volt)	VBEon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = I_C/I_B$	VA (V)	ro=VA/IC	$g_m = I_C/25mV$	$r_\pi = 25mV/I_B$
0.5	-1.5	0.37864	-0.82464	1.87864	0.67536	100	1.00E+05	1.21E-03	8.25E-06	147	55	4.53E+04	4.85E-02	3032

Figure 5: Same bias condition found in Q1

(1) How much is the measured collector current I_C in mA?

$$I_C = 1.21 * 10^{-3} A = 1.21 mA$$

(2) What are the measured V_{BEon} in volts and the base current I_B in μA ?

$$V_{BEon} = 0.67536 V, I_B = 8.25 * 10^{-6} A = 8.25 \mu A$$

(3) What is the $\beta = I_C/I_B$ value at this I_C ?

$$\beta = \frac{I_C}{I_B} = 147$$

(4) What is the early voltage $|V_A|$ in volts?

$$|V_A| = 55 V$$

(5) What is the output resistance r_o in $k\Omega$?

$$r_o = \frac{V_A}{I_C} = 4.53 * 10^4 \Omega = 45.3 k\Omega$$

(6) What is the transconductance g_m in mS?

$$g_m = \frac{I_C}{25mV} = 4.85 * 10^{-2} \frac{A}{mV} = 48.5 mS$$

(7) What is the input resistance r_{π} in $k\Omega$?

$$r_{\pi} = \frac{25mV}{I_B} = 3032 \frac{mV}{A} = 3.032 k\Omega$$

Part 2: DC Characterization of a PNP-BJT 2N3906

A) SPICE Simulation

2.1

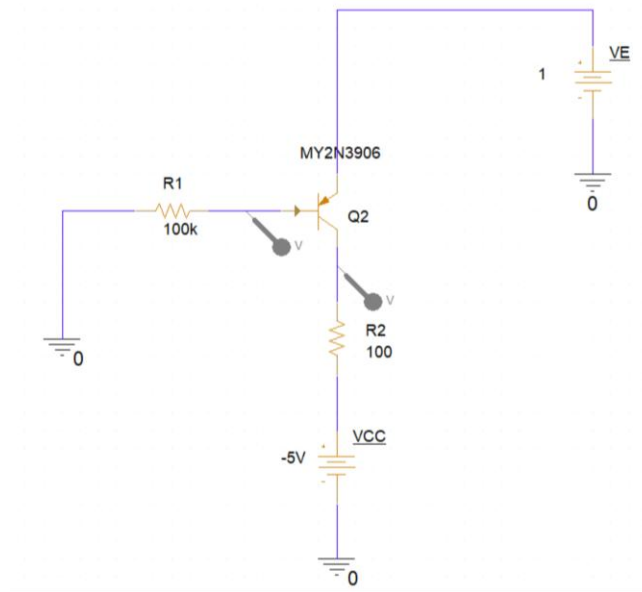


Figure 6: PSpice schematic diagram used to characterize a PNP-BJT 2N3906

2.2

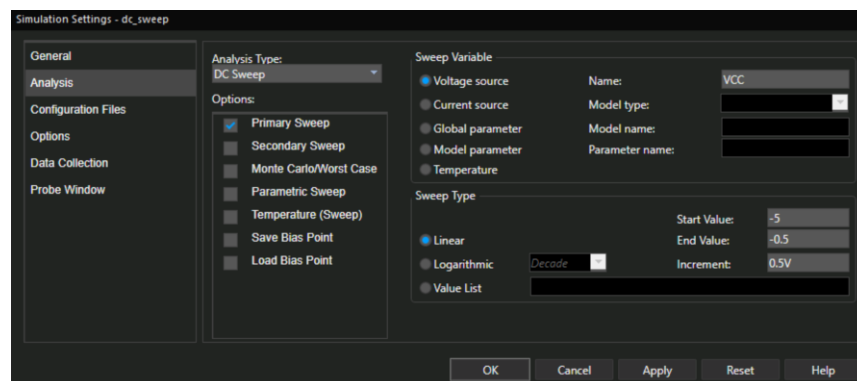


Figure 7: PSpice simulation settings used for DC sweep

2.3 The V_A represents the early voltage which is a measure of the output resistance of a BJT in the active region. By observing the definition of V_A in Fig. 6.18 of the textbook, I was able to calculate the V_A from the I_C vs. V_{CE} plot in excel using the equation of the trendline to solve for the intercept by setting $I_C = 0$:

$$I_C = mV_{CE} + b$$

$$0 = mV_{CE} + b$$

$$V_{CE} = -\frac{b}{m} \Rightarrow V_A = \frac{b}{m}$$

B) AD3 Measurement

2.5



Figure 8: Experimental setup for the DC characterization of an PNP-BJT 2N3906

C) Questions for Part 2

For the PNP-BJT 2N3906 characterized, if we want to bias this device to conduct a collector current $I_C \approx 1.0$ mA at the lowest V_{EC} value, answer the following questions.

Q3. (7 Points): Based on the simulated data in Steps 2.2-2.4, use the bias condition giving the closest I_C value to the desired collector current, find out:

V+ (VE)	V- (VCC)	V(Q1C) (Volt)	V(Q1B) (Volt)	VEC (Volt)	VEBon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = I_C/I_B$	VA (V)	ro=VA/IC	gm = IC/25mV	r π = 25mV/IB
1.5	-0.5	-0.397093315	0.839935339	1.90	0.660	100	1.00E+05	1.03E-03	8.40E-06	123	143	1.39E+05	4.12E-02	2976

Figure 9: Closest I_C to 1.0 mA at the lowest V_{CE} Value

(1) What are the simulated V_{EBon} in volts and the base current I_B in μA ?

$$V_{EBon} = 0.660 \text{ V}, I_B = 8.40 \times 10^{-6} \text{ A} = 8.40 \mu A$$

(2) What is the $\beta = I_C/I_B$ value at this I_C ?

$$\beta = \frac{I_C}{I_B} = 123$$

(3) What is the early voltage $|V_A|$ in volts?

$$|V_A| = 143 \text{ V}$$

(4) What is the output resistance r_o in $k\Omega$?

$$r_o = \frac{V_A}{I_C} = 1.39 * 10^5 \Omega = 139 \text{ k}\Omega$$

(5) What is the transconductance g_m in mS ?

$$g_m = \frac{I_C}{25mV} = 4.12 * 10^{-2} \frac{A}{mV} = 41.2 \text{ mS}$$

(6) What is the input resistance r_π in $k\Omega$?

$$r_\pi = \frac{25mV}{I_B} = 2976 \frac{mV}{A} = 2.976 \text{ k}\Omega$$

Q4. (8 Points): Based on the measured data in Step 2.8, use the same bias condition found in Q3 (or the first reliable data if that bias condition is an outlier), find out:

V+ (VE)	V- (VCC)	Channel 1 (VC)	Channel 2 (VB)	VEC (Volt)	VEBon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = I_C/I_B$	$ V_A $ (V)	$r_o = V_A/I_C$	$g_m = I_C/25mV$	$r_\pi = 25mV/I_B$
1.5	-0.5	-0.423	0.87924	1.92	0.621	100	1.00E+05	7.70E-04	8.79E-06	88	23	3.03E+04	3.08E-02	2843

Figure 10: Same bias condition found in Q3

(1) How much is the measured collector current I_C in mA ?

$$I_C = 7.70 * 10^{-4} \text{ A} = 0.77 \text{ mA}$$

(2) What are the measured V_{BEon} in volts and the base current I_B in μA ?

$$V_{BEon} = 0.621 \text{ V}, I_B = 8.79 * 10^{-6} \text{ A} = 8.79 \mu A$$

(3) What is the $\beta = I_C/I_B$ value at this I_C ?

$$\beta = \frac{I_C}{I_B} = 88$$

(4) What is the early voltage $|V_A|$ in volts?

$$|V_A| = 23 \text{ V}$$

(5) What is the output resistance r_o in $k\Omega$?

$$r_o = \frac{V_A}{I_C} = 3.03 * 10^4 \Omega = 30.3 \text{ k}\Omega$$

(6) What is the transconductance g_m in mS?

$$g_m = \frac{I_C}{25 \text{ mV}} = 3.08 * 10^{-2} \frac{\text{A}}{\text{mV}} = 30.8 \text{ mS}$$

(7) What is the input resistance r_π in $\text{k}\Omega$?

$$r_\pi = \frac{25 \text{ mV}}{I_B} = 2843 \frac{\text{mV}}{\text{A}} = 2.843 \text{ k}\Omega$$

Part 3: Design of a Current Source/Sink

Q5: (10 points) Express the base current I_B as a function of V_{BB} , R_{BB} , V_{BEon} , R_3 , V_{EE} , and β .

Q5:

$$i_B = i_e - i_c, \quad i_c = \beta i_B$$

$$i_B = i_e - \beta i_B$$

$$i_e = i_B (\beta + 1) \quad \text{①}$$

KVL around base-emitter loop:

$$V_{BB} - i_B R_{BB} - V_{BEon} - i_e R_3 - V_{EE} = 0$$

Sub in ①

$$V_{BB} - i_B R_{BB} - V_{BEon} - i_B (\beta + 1) R_3 - V_{EE} = 0$$

$$V_{BB} - i_B [R_{BB} + (\beta + 1) R_3] - V_{BEon} - V_{EE} = 0$$

$$i_B = \frac{V_{BB} - V_{BEon} - V_{EE}}{R_{BB} + R_3 (\beta + 1)}$$

Q6. (10 Points) Comparing the I_B expressions obtained in Q5 and in (3), what is the difference between these two equations? For a change ΔV_{EE} in the power supply V_{EE} , derive equations for the resulting change in the base current ΔI_B using the I_B expressions obtained in Q5 and in (3). Show that the emitter resistor R_3 reduces the change in the base current ΔI_B as a result of the change ΔV_{EE} in the power supply V_{EE} .

Q6:

Equation from Q5:

$$i_B = \frac{V_{BB} - V_{BEon} - V_{EE}}{R_{BB} + R_3 (\beta + 1)}$$

Equation (3):

$$i_B = \frac{V_{BB} - (V_{BE} + V_{BEon})}{R_{BB}}$$

$\Delta i_B + i_B = \frac{V_{BB} - V_{BEon} - (V_{EE} + \Delta V_{EE})}{R_{BB} + R_3 (\beta + 1)}$

$\Delta i_B + i_B = \frac{V_{BB} - (V_{EE} + \Delta V_{EE}) - V_{BEon}}{R_{BB}}$

The difference between the equation obtained in Q5, and the given equation (3) is that equation (3) does not include R_3 as it was set to zero. In the last question, I didn't set R_3 equal to zero, which is why $R_3 (\beta + 1)$ is present in the denominator of the equation for I_B .


$R_3 (\beta + 1)$ will always be a positive value since both β and R_3 are always positive, which means that the above equations will have the same numerator, but the equation derived from Q5 will have a slightly larger denominator than the one from equation (3). This proves that for any change ΔV_{EE} in the power supply V_{EE} , the change in the base current ΔI_B will always be less in the equation derived from Q5 as opposed to equation (3). This is proof that the emitter resistor R_3 reduces the change in the base current ΔI_B as a result of the change ΔV_{EE} in the power supply V_{EE} .

Q7. (15 points) Inserting the feedback R_3 at the emitter of the BJT not only stabilizes the I_B but also improves (or increases) the output resistance R_o of the current sink shown in Fig 6/ Fig 7 (i.e., I_o is more stable when there is a change in V_{CE}). Using a π -model for the BJT, prove that the output resistance of the current sink is $R_o = r_o + [R_3 \parallel (R_{BB} + R_\pi)][1 + g_m r_o \left(\frac{r_\pi}{R_{BB} + r_\pi} \right)]$.

Below is the proof from a π -model for the BJT that the output resistance of the current sink is $R_o = r_o + [R_3 \parallel (R_{BB} + R_\pi)][1 + g_m r_o \left(\frac{r_\pi}{R_{BB} + r_\pi} \right)]$.

Q7:

π -model for BJT:

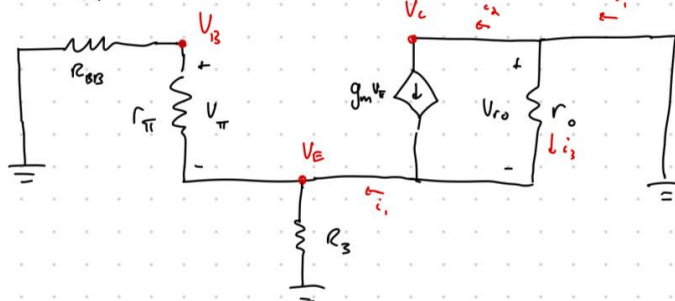

$$i_B = g_m V_\pi$$

$$i_E = i_B + i_C$$

$$= i_C + g_m V_\pi$$

$$V_{ro} = r_o i_E$$

$$V_{ro} = r_o (i_C + g_m V_\pi)$$

$$V_E = i_C \left[(R_{BB} + r_\pi) \parallel R_3 \right]$$

$$V_\pi = -V_E \cdot \frac{r_o}{R_{BB} + r_\pi}$$

$$V_C = V_E + V_{ro}$$

$$= i_C \left((R_{BB} + r_\pi) \parallel R_3 \right) + r_o (i_C + g_m V_\pi)$$

$$= i_C \left((R_{BB} + r_\pi) \parallel R_3 \right) + r_o i_C + r_o g_m V_\pi$$

$$= i_C \left((R_{BB} + r_\pi) \parallel R_3 \right) + r_o i_C + r_o g_m \left(-V_E \cdot \frac{r_\pi}{R_{BB} + r_\pi} \right)$$

$$= i_C \left((R_{BB} + r_\pi) \parallel R_3 \right) + r_o i_C + r_o \cdot \frac{g_m V_E r_\pi}{R_{BB} + r_\pi}$$

$$V_C = i_C \left((R_{BB} + r_\pi) \parallel R_3 \right) + r_o i_C + r_o \cdot \frac{g_m r_\pi}{R_{BB} + r_\pi} \cdot i_C \left((R_{BB} + r_\pi) \parallel R_3 \right)$$

$$R_o = \frac{V_C}{i_C} = \left((R_{BB} + r_\pi) \parallel R_3 \right) + i_C + r_o \cdot \frac{g_m r_\pi}{R_{BB} + r_\pi} \cdot \left((R_{BB} + r_\pi) \parallel R_3 \right)$$

$$R_o = r_o + \left((R_{BB} + r_\pi) \parallel R_3 \right) \left(1 + g_m r_o \left(\frac{r_\pi}{R_{BB} + r_\pi} \right) \right)$$

Q8. (10 Points) Inserting the feedback R_3 at the emitter of the BJT improves the stabilization of the Q-point at the cost of increased $V_{o,min}$. What is the $V_{o,min}$ of the constant current sink when $R_3 \neq 0$? Express $V_{o,min}$ as a function of I_o , which is the I_C of Q1.

Because $R_3 \neq 0$, we must consider the voltage drop when calculating the $V_{o,min}$ of the constant current sink. Below us $V_{o,min}$ expressed as a function of I_o .

Q8:

$$V_{o,min} = V_{EE} + 0.3V \quad (\text{when } R_3 = 0)$$

$$\text{Voltage drop across resistor } R_3: V_{R_3} = I_e R_3$$

$$V_{o,min} = V_{EE} + 0.3V + V_{R_3}$$

$$V_{o,min} = V_{EE} + 0.3V + I_e R_3$$

$$V_{o,min} = V_{EE} + 0.3V + \frac{\beta+1}{\beta} I_o R_3$$

Q9. (15 Points) For $V_{EE} = -5V$, if we want to design a current sink with $I_o = 1.0 \text{ mA}$ and $V_{o,min} = -1V$ using the NPN-BJT 2N3094 characterized in Q1, what is the resistance value for R_3 ? To reduce the DC power consumption of R_1 and R_2 , we usually choose large resistance values (in tens or hundreds of $k\Omega$) for R_1 and R_2 . Suppose we choose $R_2 = 100 \text{ k}\Omega$, calculate R_1 in $k\Omega$. Verify the I_o vs. V_{CC} characteristics of the design by sweeping V_{CC} from $-5V$ to $5V$ with a $0.05V$ step and post the waveform of the simulated I_o vs. V_{CC} characteristics using the command "Window -> Copy to Clipboard" in the PSpice simulator window.

Q9:

① Find R_3 :

$$V_{o,min} = V_{EE} + 0.3V + \frac{\beta+1}{\beta} I_o R_3$$

$$-1V = -5V + 0.3V + \frac{118}{117} (1mA) R_3$$

$$R_3 = \frac{-1V + 5V - 0.3V}{\frac{118}{117} (1mA)}$$

$$R_3 = 3.669 \text{ k}\Omega$$

② Find base voltage:

$$V_E = V_{EE} + I_e R_3 = -5 + \left(\frac{118}{117} \text{ mA} \right) (3.669 \text{ k}\Omega) = -1.300$$

$$V_B = V_E + V_{BE(on)} = -1.300 + 0.621$$

$$V_B = -0.679V$$

③ Solve for R_1

$$I_B R_{BB} + V_B = V_{BB}$$

$$I_B \frac{R_1 R_2}{R_1 + R_2} + V_B = \frac{R_1}{R_1 + R_2} V_{EE}$$

$$\frac{1}{11.7} \frac{100 R_1}{100 + R_1} - 0.679 = \frac{R_1}{100 + R_1} (-5)$$

$$\therefore R_1 = 13.1 \text{ k}\Omega$$

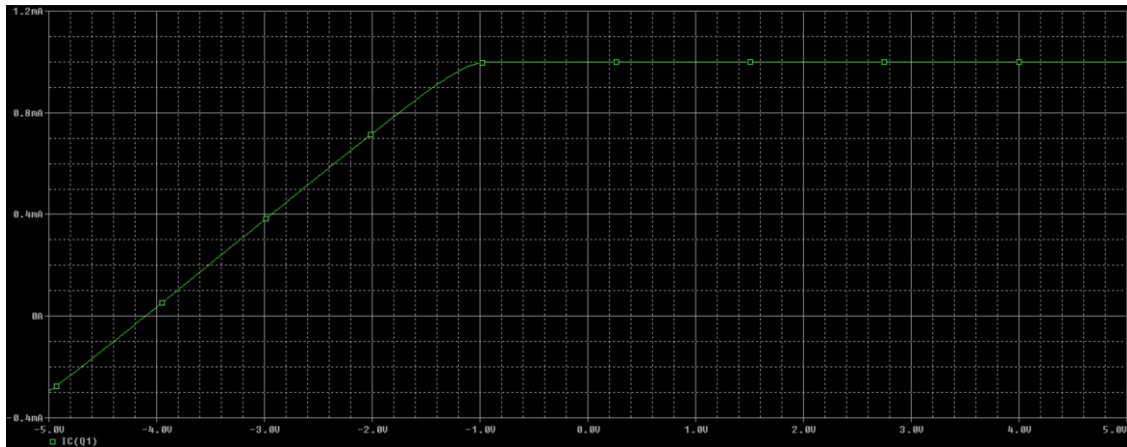


Figure 11: I_o vs. V_{CC} plot

Q10. (10 Points) When designing the constant current sink shown in Fig. 6, we assume that $|V_{CE}| \geq 0.3\text{V}$ and Q1 works in the active region. Based on the resistance values obtained in Q9, sweep V_{CC} in Fig. 6 from -5 V to $+5\text{ V}$ with a 0.05 V step and measure V_E and I_C to determine the $|V_{CE}|$ required for Q1 to work in the active region.

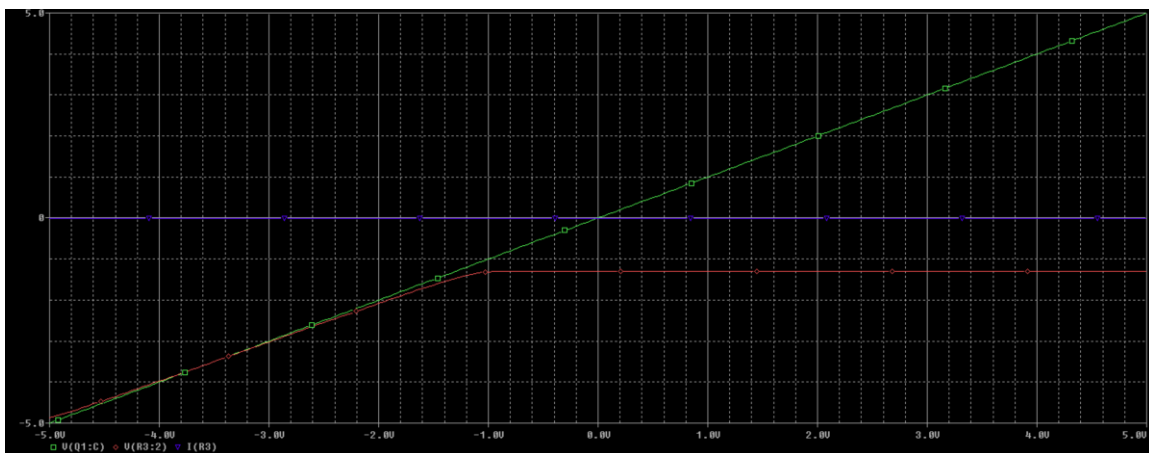


Figure 12: I_C , V_{CC} , and V_E plot

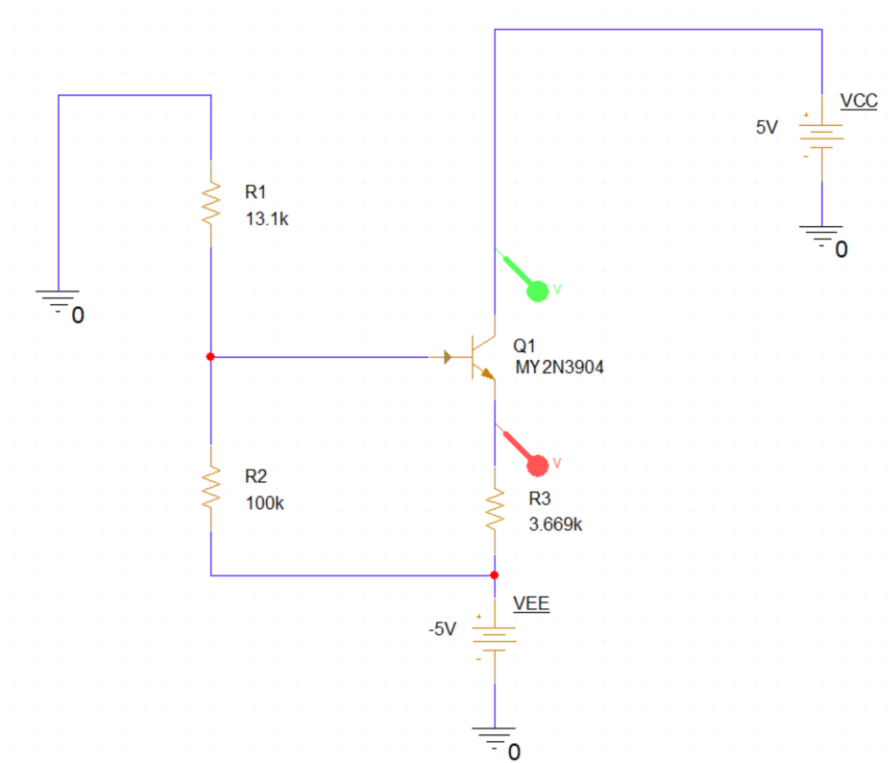


Figure 13: PSpice circuit used

From the graph that shows V_{CC} vs V_E , we can determine the $|V_{CE}|$ required for Q1 to operate in the active region. It can be observed that $|V_{CE}| = V_{cc} - V_E = (-1V) - (-1.3V) = 0.3V$. This verifies the operating condition is $|V_{CE}| \geq 0.3V$ for Q1 to work in the active region.